
 


Clk 400 MHz


TOP LEVEL DIAGRAM

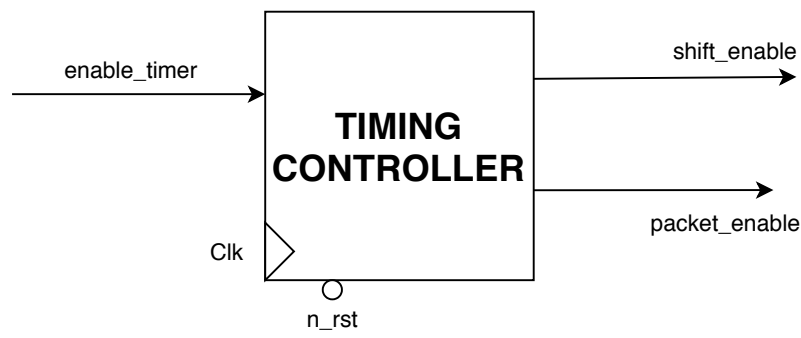

Top level



Lower Level

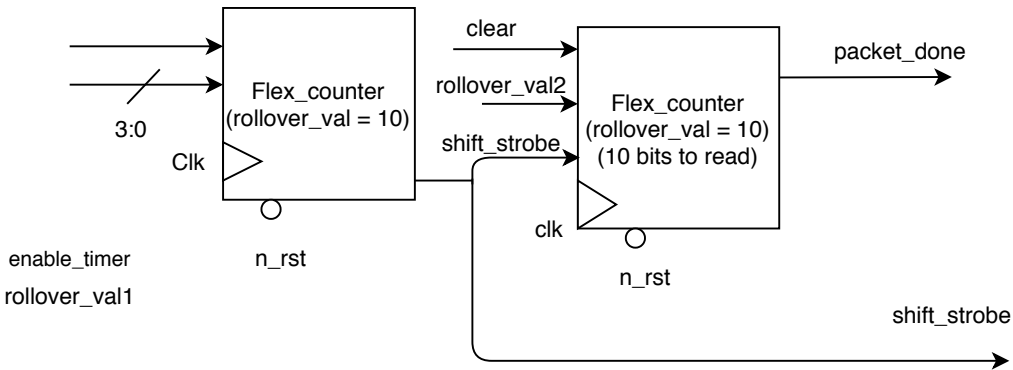

next state logic for First flex counter

```

if !enable_timer:
    next_count_out = 7
    next_shift_strobe = 0

else {
    if (count_out == 9)
        next_shift_strobe = 1
        next_count_out = count_out + 1
    else if(count_out == rollover_val1)
        next_count_out = 1
        next_shift_strobe = 0

    else:
        next_count_out = count_out1 + 1
        next_shift_strobe = 0
}

```

next state logic for Second Flex Counter

```

if clear:
    next_count = 0

else if !shift_strobe:
    next_count = count

else {
    if shift_strobe == 1
        next_count = count + 1
    else
        next_count = count
}

```

output logic for second Flex Counter

```


if count == 10
    packet_done = 1

else
    packet_done = 0

```


Receiver Control Unit (RCU)

Top Level Diagram

 

FSM TRANSITION DIAGRAM - {framing_error, packet_done, new_packet_detected}

